


## Problem 17

Consider an electric circuit containing a capacitor, resistor, and battery; see Figure 1.2.3. The charge  $Q(t)$  on the capacitor satisfies the equation<sup>5</sup>

$$R \frac{dQ}{dt} + \frac{Q}{C} = V,$$

where  $R$  is the resistance,  $C$  is the capacitance, and  $V$  is the constant voltage supplied by the battery.

- If  $Q(0) = 0$ , find  $Q(t)$  at any time  $t$ , and sketch the graph of  $Q$  versus  $t$ .
- Find the limiting value  $Q_L$  that  $Q(t)$  approaches after a long time.
- Suppose that  $Q(t_1) = Q_L$  and that at time  $t = t_1$  the battery is removed and the circuit is closed again. Find  $Q(t)$  for  $t > t_1$  and sketch its graph.

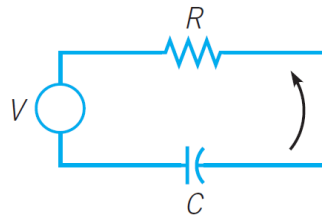

**FIGURE 1.2.3** The electric circuit of Problem 17.

---

<sup>5</sup>This equation results from Kirchhoff's laws, which are discussed in Section 3.7.