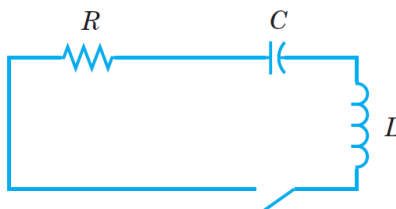


## Problem 12

A series circuit has a capacitor of  $10^{-5}$  F, a resistor of  $3 \times 10^2 \Omega$ , and an inductor of 0.2 H. The initial charge on the capacitor is  $10^{-6}$  C and there is no initial current. Find the charge  $Q$  on the capacitor at any time  $t$ .

### Solution

Start by drawing an RLC series circuit.



Assume that the circuit is closed at  $t = 0$ . Apply Faraday's law to obtain the governing ODE for the current.

$$\sum V = -L \frac{di}{dt}$$

The only potential drops occur over the resistor and the capacitor.

$$iR + \frac{q}{C} = -L \frac{di}{dt}$$

Write  $i = dq/dt = q'$ .

$$Rq' + \frac{q}{C} = -Lq''$$

Bring  $Lq''$  to the left side and divide both sides by  $L$ .

$$q'' + \frac{R}{L}q' + \frac{1}{LC}q = 0 \quad (1)$$

Since the coefficients are constant and this is a homogeneous ODE, the solutions are of the form  $q = e^{rt}$ .

$$q = e^{rt} \rightarrow q' = re^{rt} \rightarrow q'' = r^2e^{rt}$$

Substitute these expressions to obtain an algebraic equation for  $r$ .

$$r^2e^{rt} + \frac{R}{L}(re^{rt}) + \frac{1}{LC}(e^{rt}) = 0$$

Divide both sides by  $e^{rt}$ .

$$r^2 + \frac{R}{L}r + \frac{1}{LC} = 0$$

$$r = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2} = \frac{-1500 \pm \sqrt{250000}}{2} = \frac{-1500 \pm 500}{2} = -750 \pm 250$$

$$r = \{-1000, -500\}$$

Two solutions to equation (1) are then  $q = e^{-1000t}$  and  $q = e^{-500t}$ . By the principle of superposition, the general solution is a linear combination of these two.

$$q(t) = C_1e^{-1000t} + C_2e^{-500t}$$

Take a derivative of it with respect to  $t$ .

$$q'(t) = -1000C_1e^{-1000t} - 500C_2e^{-500t}$$

Now apply the initial conditions,  $q(0) = 10^{-6}$  and  $q'(0) = 0$ , to determine  $C_1$  and  $C_2$ .

$$\begin{aligned}q(0) &= C_1 + C_2 = 10^{-6} \\q'(0) &= -1000C_1 - 500C_2 = 0\end{aligned}$$

Solving this system of equations yields  $C_1 = -10^{-6}$  and  $C_2 = 2 \times 10^{-6}$ . Therefore,

$$q(t) = -10^{-6}e^{-1000t} + 2 \times 10^{-6}e^{-500t}.$$

Note that the charge  $q(t)$  is in Coulombs (C).

