

## Problem 8

A series circuit has a capacitor of  $0.25 \times 10^{-6}$  F and an inductor of 1 H. If the initial charge on the capacitor is  $10^{-6}$  C and there is no initial current, find the charge  $Q$  on the capacitor at any time  $t$ .