

### Exercise 7.2.1

From Kirchhoff's law the current  $I$  in an  $RC$  (resistance-capacitance) circuit (Fig. 7.1) obeys the equation

$$R \frac{dI}{dt} + \frac{1}{C} I = 0.$$

- (a) Find  $I(t)$ .
- (b) For a capacitance of  $10,000 \mu\text{F}$  charged to  $100 \text{ V}$  and discharging through a resistance of  $1 \text{ M}\Omega$ , find the current  $I$  for  $t = 0$  and for  $t = 100$  seconds.

*Note.* The initial voltage is  $I_0 R$  or  $Q/C$ , where  $Q = \int_0^\infty I(t) dt$ .

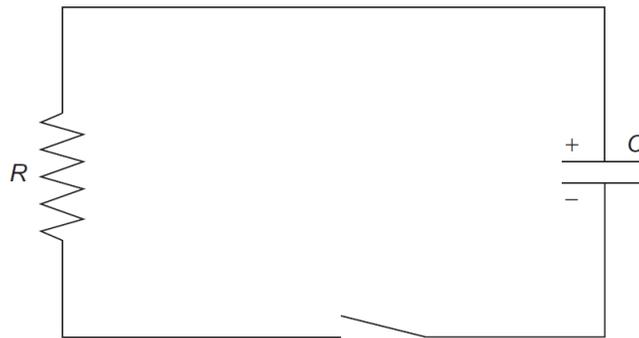


FIGURE 7.1 RC circuit.

### Solution

#### Part (a)

$$RI' + \frac{1}{C}I = 0$$

Bring the second term to the right side.

$$RI' = -\frac{1}{C}I$$

Divide both sides by  $RI$ .

$$\frac{I'}{I} = -\frac{1}{RC}$$

The left side can be written as  $d/dt(\ln I)$  by the chain rule.

$$\frac{d}{dt}(\ln I) = -\frac{1}{RC}$$

Integrate both sides with respect to  $t$ .

$$\ln I = -\frac{t}{RC} + C_1$$

Exponentiate both sides.

$$\begin{aligned} I(t) &= e^{-t/RC + C_1} \\ &= e^{C_1} e^{-t/RC} \end{aligned}$$

Use a new constant  $A$  for  $e^{C_1}$ .

$$I(t) = Ae^{-t/RC}$$

**Part (b)**

Use the relationship between voltage and charge for a capacitor to determine  $A$ .

$$\begin{aligned} V &= \frac{Q}{C} \\ &= \frac{1}{C} \int_0^\infty I(t) dt \\ &= \frac{1}{C} \int_0^\infty Ae^{-t/RC} dt \\ &= \frac{A}{C}(-RC)(0 - 1) \\ &= AR \end{aligned}$$

Consequently,

$$A = \frac{V}{R} = \frac{100 \text{ V}}{10^6 \Omega} = 0.0001 \text{ amps}$$

and

$$I(t) = 0.0001 \exp\left(-\frac{t}{10000}\right).$$

Therefore,

$$\begin{aligned} I(0) &= 0.0001 \text{ amps} \\ I(100) &\approx 0.000099 \text{ amps.} \end{aligned}$$

The graph below shows  $I(t)$  vs.  $t$ , the charge on the capacitor as a function of time.

