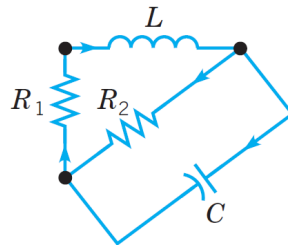


## Problem 21

Consider the circuit shown in Figure 7.1.5. Use the method outlined in Problem 19 to show that the current  $I$  through the inductor and the voltage  $V$  across the capacitor satisfy the system of differential equations


$$L \frac{dI}{dt} = -R_1 I - V, \quad C \frac{dV}{dt} = I - \frac{V}{R_2}.$$



**FIGURE 7.1.5** The circuit in Problem 21.

### Solution

Label the circuit as shown below.

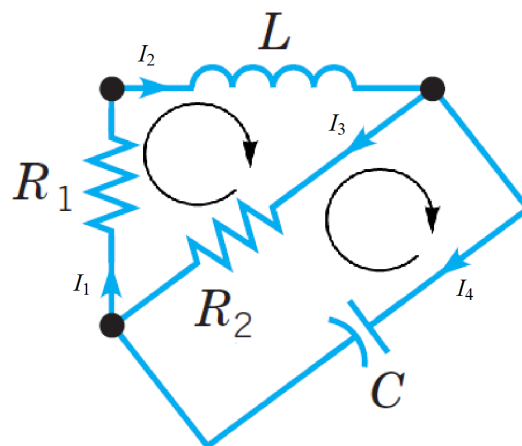

Apply Kirchhoff's voltage law (KVL) to the two clockwise loops. All currents go in the direction of the arrows except for  $I_3$ .

$$\text{Left:} \quad \sum V_i = 0 \quad \rightarrow \quad +V_1 + V_2 + V_3 = 0$$

$$\text{Right:} \quad \sum V_i = 0 \quad \rightarrow \quad -V_3 + V_4 = 0$$

Apply Kirchhoff's current law (KCL) to the three nodes. Whether a current is positive or negative depends if it goes into or out of a node.

$$I_1 - I_2 = 0$$

$$I_3 + I_4 - I_1 = 0$$

$$I_2 - I_3 - I_4 = 0$$

Since  $I_1 = I_2$ , the second and third equations are identical. The current through the inductor and the voltage across the capacitor are the quantities of interest, so  $V_4 = V$  and  $I_2 = I$ .

$$V = V_3 \tag{1}$$

$$V_3 = -V_1 - V_2 \tag{2}$$

$$I = I_1 \tag{3}$$

$$I = I_3 + I_4 \tag{4}$$

The voltage-current relations for the different circuit elements are as follows.

$$\text{Capacitor: } V = \frac{Q}{C} \quad \Rightarrow \quad \frac{dV_4}{dt} = \frac{I_4}{C}$$

$$\text{Resistor: } V = IR \quad \Rightarrow \quad V_3 = I_3 R_2 \quad V_1 = I_1 R_1$$

$$\text{Inductor: } V = L \frac{dI}{dt} \quad \Rightarrow \quad V_2 = L \frac{dI_2}{dt}$$

With  $I = I_2 = I_1$  and these formulas for  $V_1$  and  $V_2$ , equation (2) becomes

$$V = -IR_1 - L \frac{dI}{dt},$$

or

$$\boxed{L \frac{dI}{dt} = -R_1 I - V.}$$

Since  $V_3 = V_4 = V$  and  $I_3 = V/R_2$ , equation (4) becomes

$$I = \frac{V}{R_2} + C \frac{dV}{dt},$$

or

$$\boxed{C \frac{dV}{dt} = I - \frac{V}{R_2}.}$$